

# **CS3350B**

# **Computer Architecture**

**Winter 2015**

## **Lecture 5.4: Combinational Logic Blocks**


**Marc Moreno Maza**

[www.csd.uwo.ca/Courses/CS3350b](http://www.csd.uwo.ca/Courses/CS3350b)

[Adapted from lectures on  
*Computer Organization and Design*,  
Patterson & Hennessy, 5<sup>th</sup> edition, 2013]
 
# Review


- Use this table and techniques we learned to transform from 1 to another



# Plan


- **Data Multiplexors**
- **Arithmetic and Logic Unit**
- **Adder/Subtractor**
 
# Data Multiplexor (here 2-to-1, n-bit-wide)



# N instances of 1-bit-wide mux

How many rows in TT?

 


---

$$\begin{aligned}c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\ &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\ &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\ &= \bar{s}(a(1) + s((1)b) \\ &= \bar{s}a + sb\end{aligned}$$




# How do we build a 1-bit-wide mux?

$$\bar{s}a + sb$$

 

# 4-to-1 Multiplexor?


How many rows in TT?

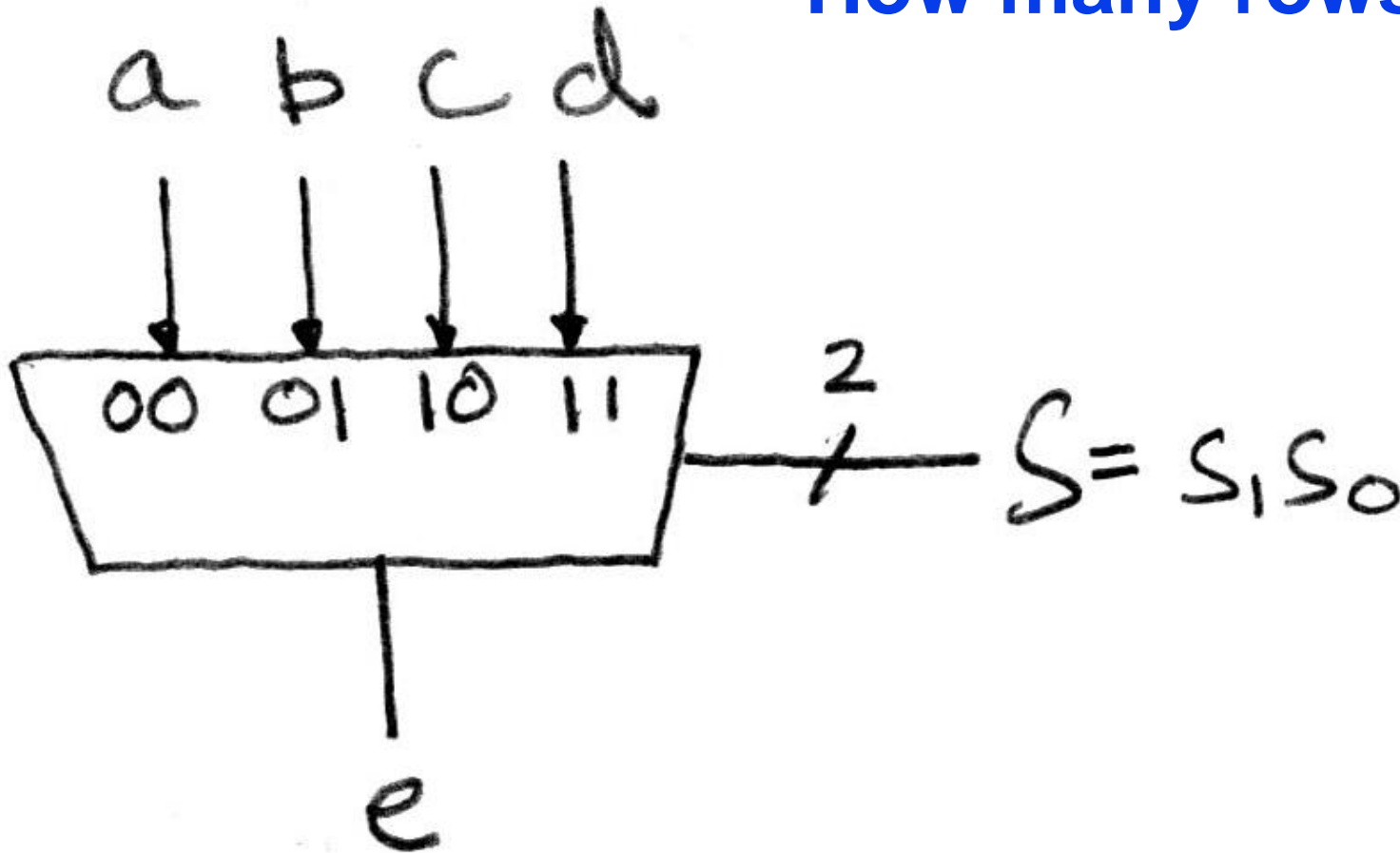

$$e = \bar{s}_1\bar{s}_0a + \bar{s}_1s_0b + s_1\bar{s}_0c + s_1s_0d$$

Is there any other way to do it?

Hint: NCAA tourney!

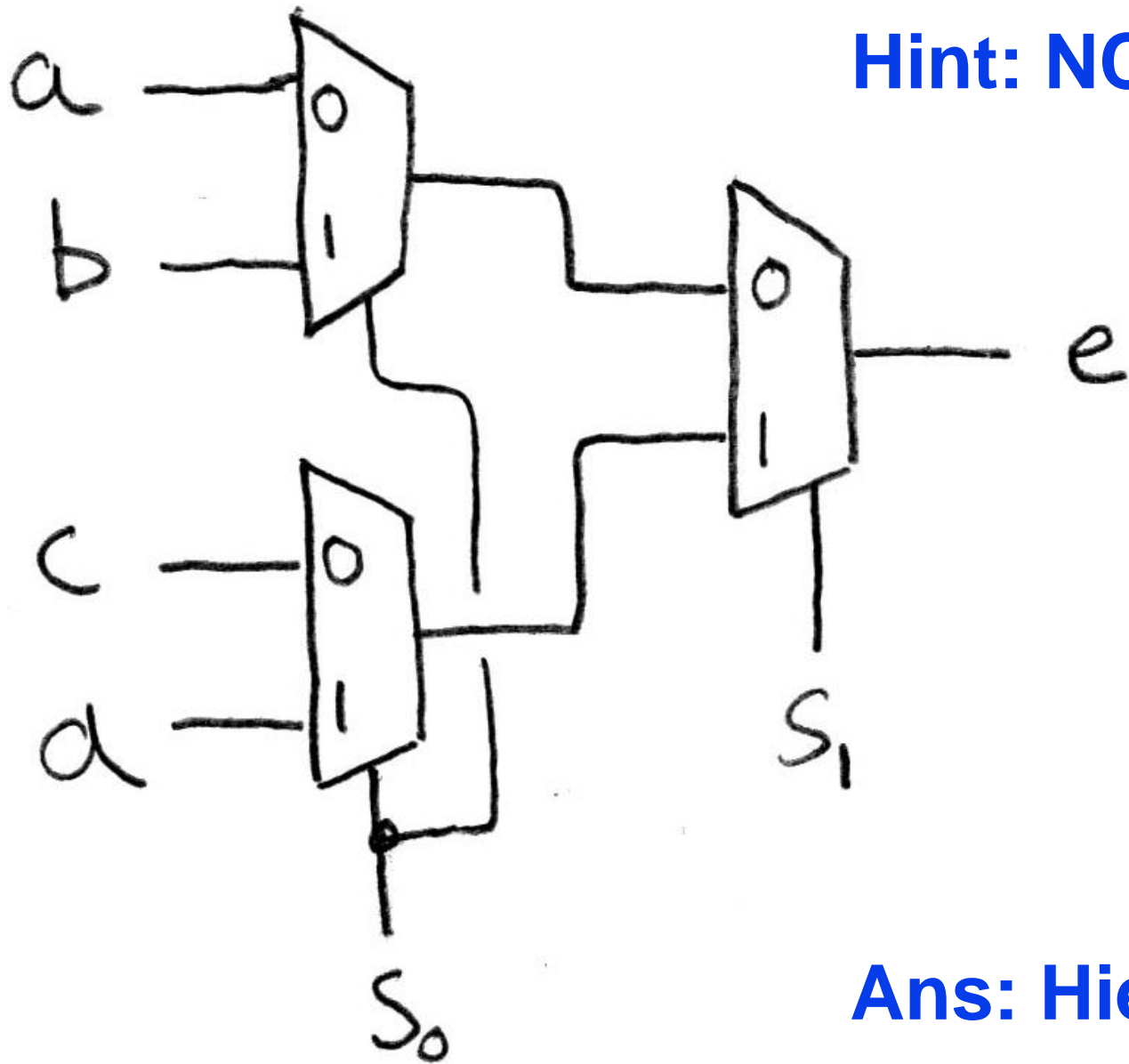


Ans: Hierarchically!


 
# Arithmetic and Logic Unit

- Most processors contain a special logic block called “Arithmetic and Logic Unit” (ALU)
- We’ll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR




when  $S=00$ ,  $R=A+B$

when  $S=01$ ,  $R=A-B$

when  $S=10$ ,  $R=A \text{ AND } B$

when  $S=11$ ,  $R=A \text{ OR } B$

# Our simple ALU

 

# Adder/Subtractor Design -- how?

- **Truth-table, then determine canonical form, then minimize and implement as we've seen before**
- **Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer**

# Adder/Subtractor – One-bit adder LSB...

$$\begin{array}{rcccc} & \mathbf{a_3} & \mathbf{a_2} & \mathbf{a_1} & \mathbf{a_0} \\ + & \mathbf{b_3} & \mathbf{b_2} & \mathbf{b_1} & \mathbf{b_0} \\ \hline \mathbf{s_3} & \mathbf{s_2} & \mathbf{s_1} & \mathbf{s_0} & \end{array}$$

$\mathbf{a_0}$	$\mathbf{b_0}$	$\mathbf{s_0}$	$\mathbf{c_1}$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$



# Adder/Subtractor – One-bit adder (1/2)...

				$a_i$	$b_i$	$c_i$	$S_i$	$C_{i+1}$
				0	0	0	0	0
				0	0	1	1	0
				0	1	0	1	0
+	$a_3$	$a_2$	$a_1$	$a_0$	0	1	0	1
	$b_3$	$b_2$	$b_1$	$b_0$	0	1	1	0
	$s_3$	$s_2$	$s_1$	$s_0$	1	0	1	0
				1	0	1	0	1
				1	1	0	0	1
				1	1	1	1	1

$$S_i =$$


$$C_{i+1} =$$
  
# Adder/Subtractor – One-bit adder (2/2)...



$$s_i = \text{XOR}(a_i, b_i, c_i)$$
$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$
 
# N 1-bit adders $\Rightarrow$ 1 N-bit adder




**What about overflow?**  
**Overflow =  $c_n$ ?**
 
# What about overflow?

- Consider a 2-bit signed # & overflow:

- 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



- Highest adder

- $C_1 = \text{Carry-in} = C_{in}$ ,  $C_2 = \text{Carry-out} = C_{out}$
- No  $C_{out}$  or  $C_{in} \Rightarrow \text{NO overflow!}$

What op? •  $C_{in}$ , and  $C_{out} \Rightarrow \text{NO overflow!}$


- $C_{in}$ , but no  $C_{out} \Rightarrow A, B \text{ both } > 0, \text{ overflow!}$
- $C_{out}$ , but no  $C_{in} \Rightarrow A, B \text{ both } < 0, \text{ overflow!}$



# What about overflow?

- Consider a 2-bit signed # & overflow:

10	=	-2
11	=	-1
00	=	0
01	=	1

 


- Overflows when...

- $C_{in}$ , but no  $C_{out} \Rightarrow A, B$  both  $> 0$ , overflow!
- $C_{out}$ , but no  $C_{in} \Rightarrow A, B$  both  $< 0$ , overflow!

$$\text{overflow} = C_n \text{ XOR } C_{n-1}$$

# Extremely Clever Subtractor

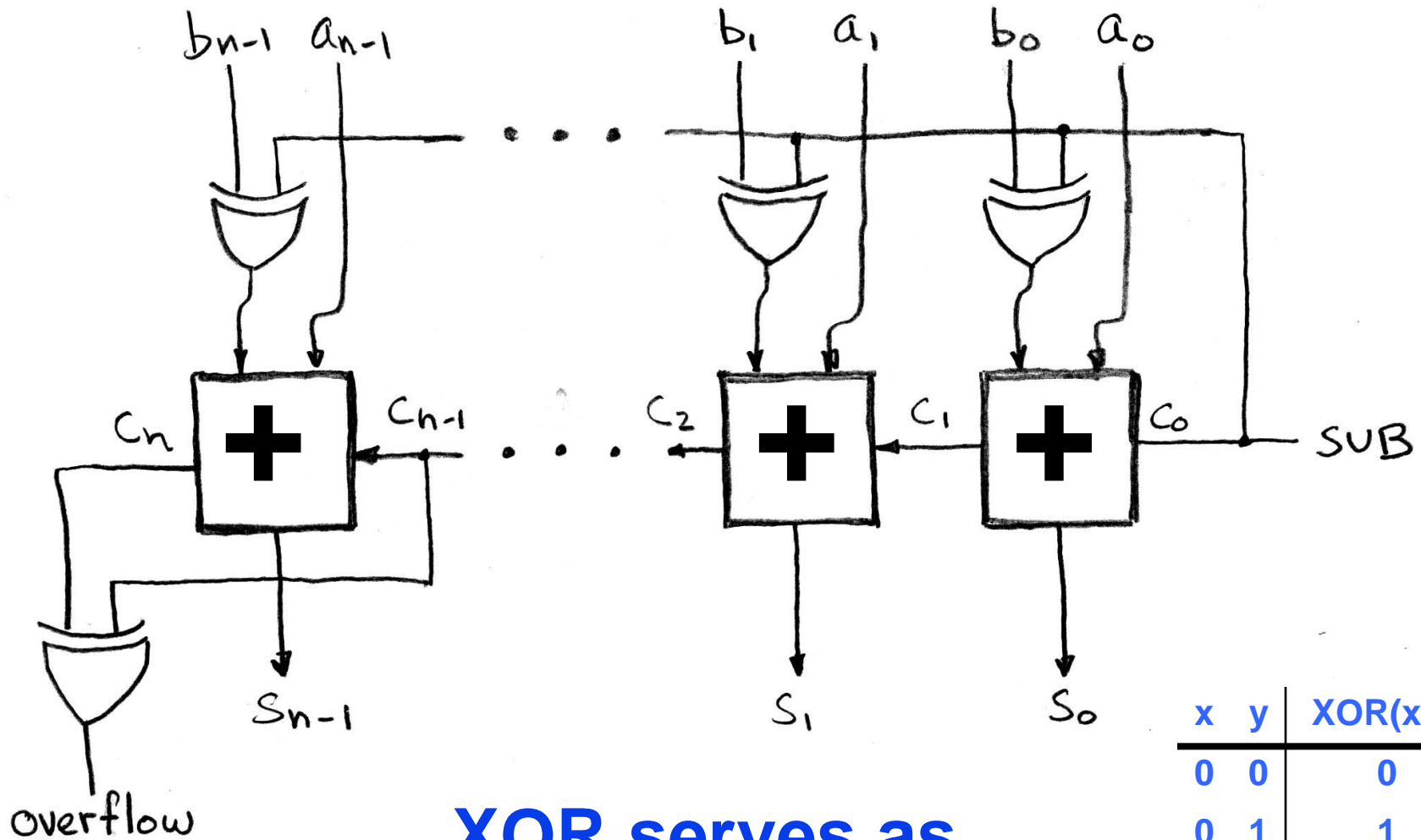

**XOR serves as  
conditional inverter!**

x	y	XOR(x,y)
0	0	0
0	1	1
1	0	1
1	1	0

## “And In conclusion...”

- **Use muxes to select among input**
  - **S input bits selects  $2^S$  inputs**
  - **Each input can be n-bits wide, indep of S**
- **Can implement muxes hierarchically**
- **ALU can be implemented using a mux**
  - **Coupled with basic block elements**
- **N-bit adder-subtractor done using N 1-bit adders with XOR gates on input**
  - **XOR serves as conditional inverter**